

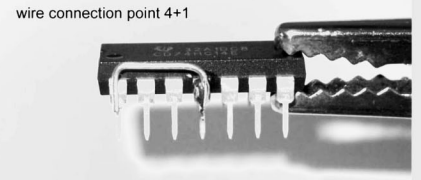
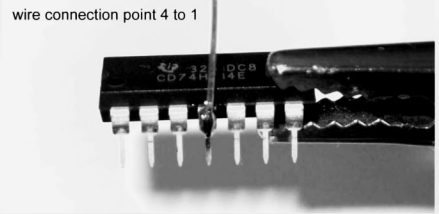



IC

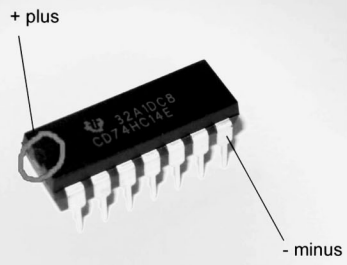


all wire connections Point 1+4
6+9
11+14

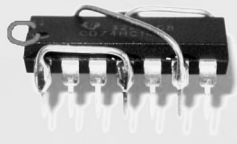


all wire connections Point 1+4
6+9
11+14

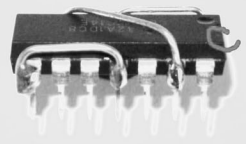

all wire connections

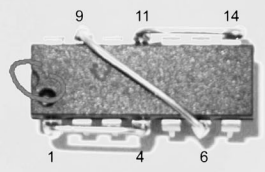

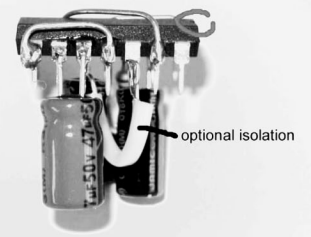3 Capacitors point 2+3 point 5+10 point 12+13



3 Capacitors point 2+3 point 5+10 point 12+13




3 Resistors point 3+4 point 5+6 point 13+14



3 Resistors point 3+4 point 5+6 point 13+14



small cross = positiv

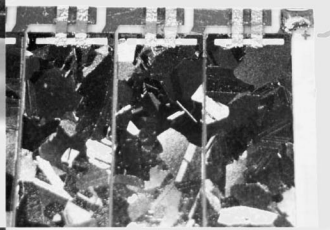


Red wire +


White wire-



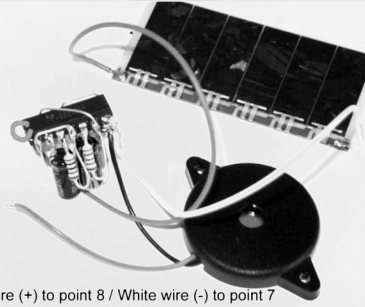Red wire (+) to point 8 / White wire (-) to point 7
Black wire (Piezospeaker) also to point 7



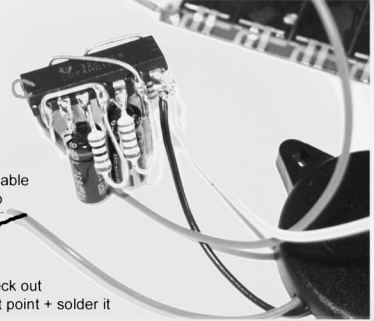red cable piezo
first check out the best point + solder it



complete solar sound modul

